

Using LTspice - a Short Intro


LTspice, also called SwitcherCAD, is a powerful and easy to use schematic capture program and SPICE engine, which is a general-purpose circuit simulation program for nonlinear DC, nonlinear transient, and linear AC analysis. LTspice authored by Mike Engelhardt can be downloaded for free at

<https://www.analog.com/en/design-center/design-tools-and-calculators/ltspice-simulator.html>

On the left side there are several downloads

- the program itself, you must run the LTspiceXVII.exe program to install the software
- user guide
- getting started

1. Example of a simple DC analysis

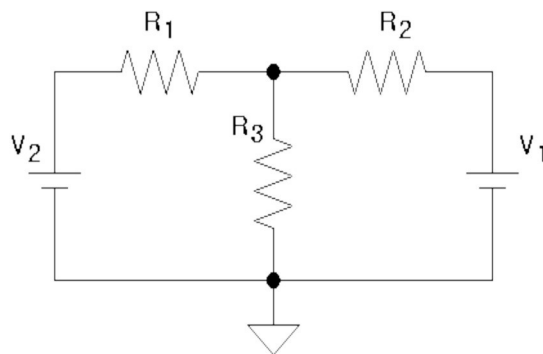

The values of components are:


$V_1 = 5V$
 $V_2 = 10V$
 $R_1 = 10$
 $R_2 = 20$
 $R_3 = 5$



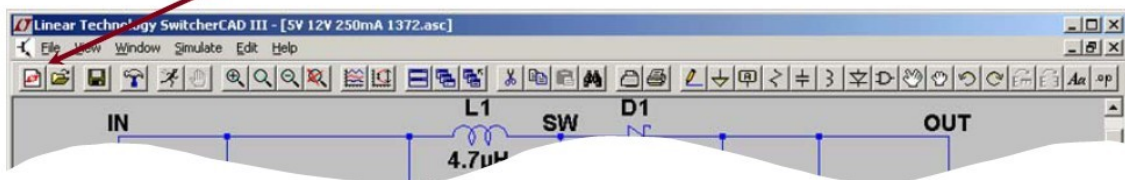
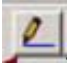
Goal: determine the current flowing through each resistor and voltages of nodes.


Step 1. Draw the circuit.

Go to File -> New schematic to create a new circuit.


New Schematic



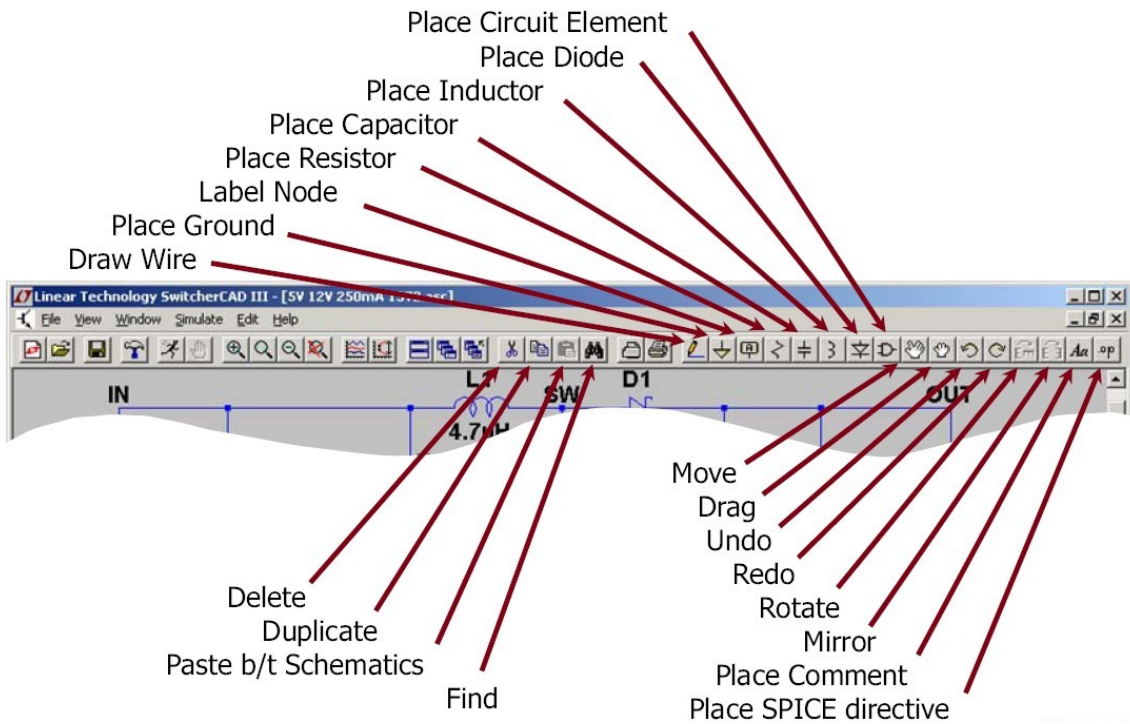Select the components from the Schematic Editor Toolbar. In this example, you'll need three resistors , two DC voltages (select Component , type voltage and hit ok), a ground , and wires connecting the components . By default, components are placed vertically, so you may want to rotate two resistors. You can do so by typing Ctrl-R while moving the elements in order to place them wherever you want.




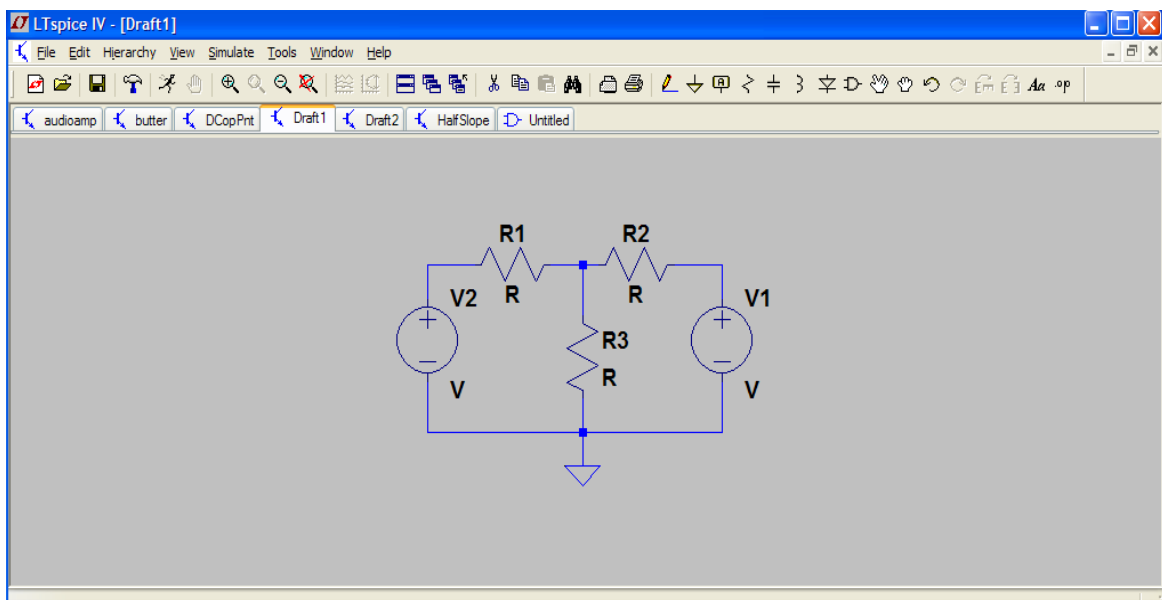Once you are done your circuit should look like this. Note that you can zoom in/out by scrolling.




Step 2. Enter the values.

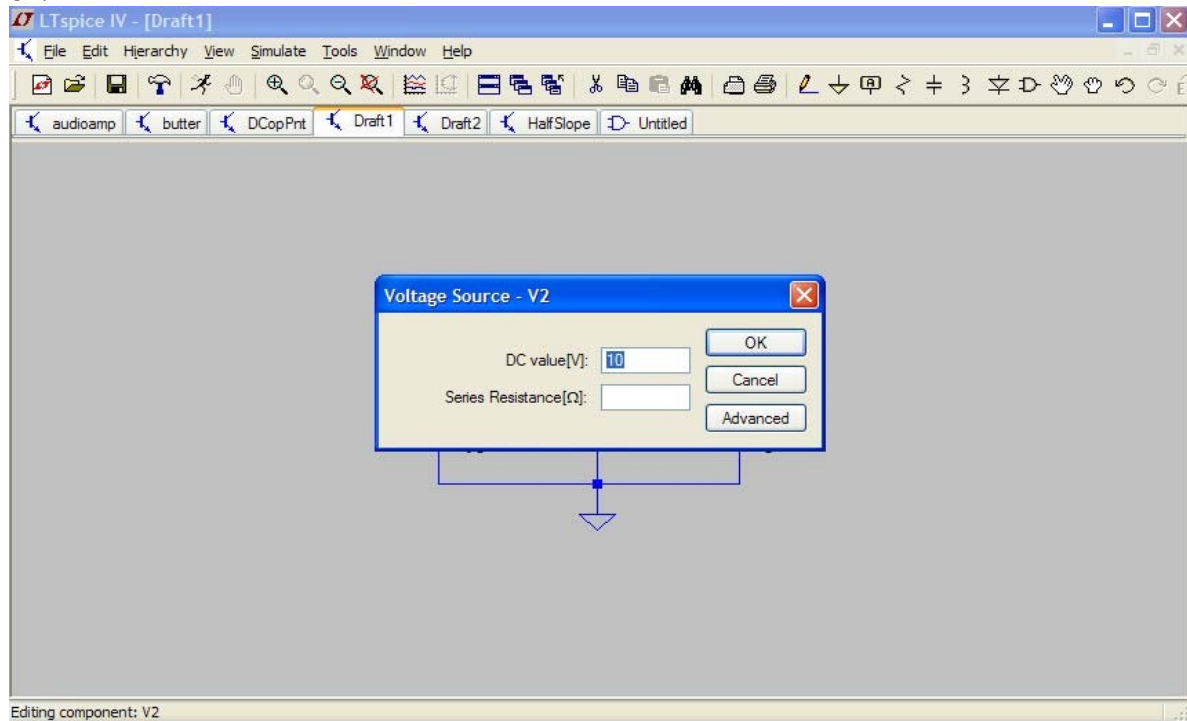Right click on each component. A window will pop up like this. Enter the value and hit ok.



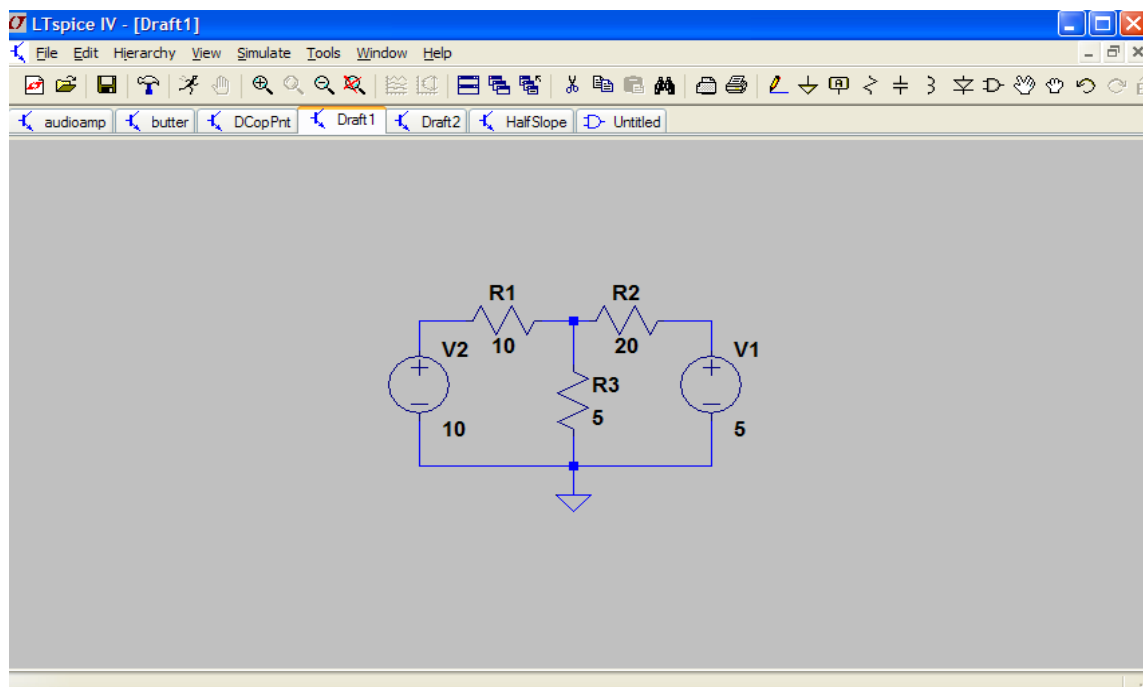Finally, your circuit diagram should look like this.



Step 3 Go to Simulate > OK  or hit F5.

Result will be shown in a pop-up window.

--- Operating Point ---

V(n002):	3.57143	voltage
V(n001):	10	voltage
V(n003):	5	voltage
I(R3):	0.714286	device_current
I(R2):	0.0714286	device_current
I(R1):	-0.642857	device_current
I(V2):	-0.642857	device_current
I(V1):	-0.0714286	device_current